

Physics Unit: DC Circuits


Worksheet 4: Combination Circuits

Review:

1. Three 100-Ω resistors are connected in series to a 12 volt battery.
 - a. What is the total resistance of the circuit? 300Ω
 - b. What current runs out of the battery? $\frac{12}{300} = \frac{1}{25} = 0.04A$
 - c. What current runs through each resistor? $0.04A$
 - d. What is the voltage across each resistor? $4V$

2. Three 100-Ω resistors are connected in parallel to a 12 volt battery.
 - a. What is the total resistance of the circuit? $\frac{1}{\frac{1}{100} + \frac{1}{100} + \frac{1}{100}} = \frac{3}{100} = \frac{1}{33.3} \Rightarrow R = 33.3\Omega$
 - b. What current runs out of the battery? $\frac{12}{33.3} = I = 0.36A$
 - c. What current runs through each resistor? $= 0.12A$
 - d. What is the voltage across each resistor? $12V$

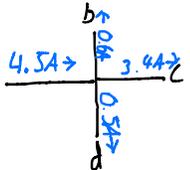
3. Four wires (A, B, C and D) come together in a junction. Wire A carries a current of 4.5 amps towards the wire while wire B carries a current of 6.0 amps away from the junction. If wire C carries a current of 3.4 amps away from the junction then what is the current through wire D? $4.5 - 0.6 - 3.4 = 0.5A$



4. A 12-volt battery is connected to three resistors (R_1 , R_2 and R_3) in series. R_1 is 400 Ω and R_2 is 300 Ω. If the current coming out of the battery is 0.01 amps, what is the value of R_3 ?

$V = IR \Rightarrow R = \frac{V}{I} = \frac{12}{0.01} = 1200$
 $SR = 1200 = 400 + 300 + R_3 \Rightarrow R_3 = 500\Omega$
 $\frac{1}{30} + \frac{1}{60} = \frac{2}{60} + \frac{1}{60} = \frac{3}{60} = \frac{1}{20} \Rightarrow R = 20\Omega$

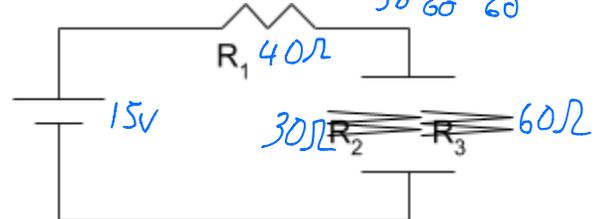
5. In the circuit to the right, the resistances are $R_1 = 40 \Omega$, $R_2 = 30 \Omega$ and $R_3 = 60 \Omega$. The voltage of the battery is 1.5 volts.




- a. What is the net resistance of the circuit? 60Ω
- b. What is the current from the battery? $\frac{1.5}{60} = \frac{1}{40} = 0.025A$
- c. Rank the resistors in terms of the amount of current from the one with the greatest current to the one with the least (including ties). $40\Omega, 30\Omega, 60\Omega$

$\frac{1}{60} + \frac{1}{120} = \frac{2}{120} + \frac{1}{120} = \frac{3}{120} = \frac{1}{40} \Rightarrow R = 40\Omega$

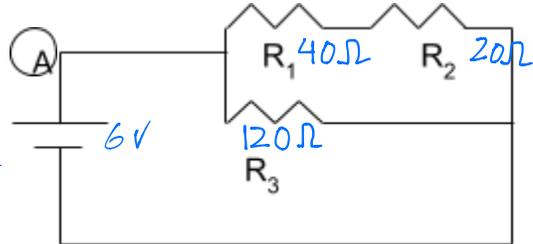6. In the circuit to the right, the resistances are $R_1 = 40 \Omega$, $R_2 = 20 \Omega$ and $R_3 = 120 \Omega$. The voltage of the battery is 6 volts.



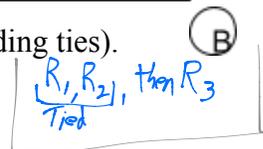- a. What is the net resistance of the circuit? 40Ω
- b. What is the current from the battery? $\frac{6}{40} = 0.15A$
- c. Rank the resistors in terms of the amount of current from the one with the greatest current to the one with the least (including ties).
- d. What is the electric potential at point A? $6V$
- e. What is the electric potential at point B? $0V$
- f. What is the potential difference across R_3 ? $6V$
- g. What is the voltage across the R_1, R_2 branch of the circuit? $6V$



Continued on next page


7. Use the circuit to the right to answer the following questions.

a. Find the total resistance of this circuit = 15Ω

b. What current runs out of the battery? $I = 0.4A$

c. What is the potential at points A, B, C and D?
 $V_A = 6V$, $V_B = 6 - 1.6 = 4.4V$,
 $V_C = 4.4 - 0.8 = 3.6V$, $V_D = 3.6 - 3.6 = 0$

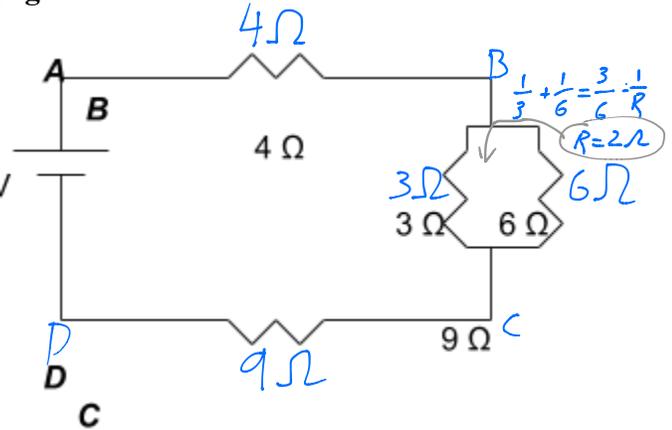d. Find the voltage across and current through each resistor in this circuit. (You might not do them in this order. I wouldn't.)



$V_{4\Omega} = 1.6V$ $V_{3\Omega} = 0.8V$ $V_{6\Omega} = 0.8V$ $V_{9\Omega} = 3.6V$

$I_{4\Omega} = 0.4A$ $I_{3\Omega} = 0.267A$ $I_{6\Omega} = 0.133A$ $I_{9\Omega} = 0.4A$

$P_{4\Omega} = 0.64W$ $P_{3\Omega} = 0.213W$ $P_{6\Omega} = 0.107W$ $P_{9\Omega} = 1.44W$

8. Use the circuit to the right to answer the following questions.

a. Find the total resistance of this circuit. $160 + 40 + 200 = 400\Omega$

b. If this circuit draws a current of 0.015 A, what is the voltage of the battery?
 $V = IR = 0.015 \cdot 400$ $V = 6V$

c. What is the equivalent resistance between points A and B?

160Ω

d. What is the total current running from point A to B?
 $0.015A$

e. What is the potential at points A, B, C and D?
 $V_A = 6V$, $V_B = 3 + 40 \cdot 0.015 = 3.6V$, $V_C = 0.015 \cdot 200 = 3V$, $V_D = 0V$

f. What is the potential difference (including a sign) in going from point A to B? B to C? C to D? D to A?

$-2.4V$ $-0.6V$ $-3V$ $+6V$

g. What is the current through the 40 Ω resistor?

$0.015A$

